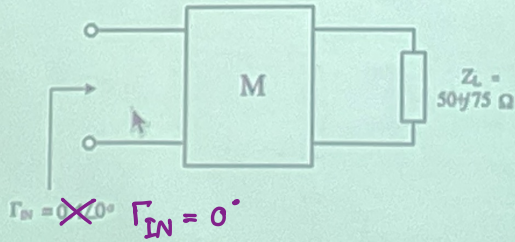


## QUIZ 2

Design the matching circuit M at the operating frequency of 2.4 GHz by using transmission line and stub matching. (50 ohm system)



Please submit to classroom  
January 10, 2023 (7 pm)

นางสาว โสภณ

สุวิมลวรรณ

620101631188

Sec.1 Commu Cir  
Design

(PAK)

$$Z_{in} = 50 \Omega, \quad z_{in} = \frac{Z_{in}}{Z_0} = \frac{50 \Omega}{50 \Omega} = 1 \rightarrow y_{in} = 1$$


$$z_L = \frac{Z_L}{Z_0} = \frac{50 + j75}{50} = 1 + j1.5 \rightarrow y_L = 0.31 - j0.46$$

$$jX_L = (1 + j1.5) - (1 - j1.5) = j3 \xrightarrow{\text{Denormalised}} jX_L = j3(50) = j150$$

$$jX_C = (1 + j0) - (1 - j1.5) = j1.5 \rightarrow jX_C = j1.5(50) = j75$$

$$C_{\text{series}} = \frac{b}{2\pi f Z_0} = \frac{1.5}{2\pi(2.4 \times 10^9)(50)} = 1.989 \text{ pF}$$
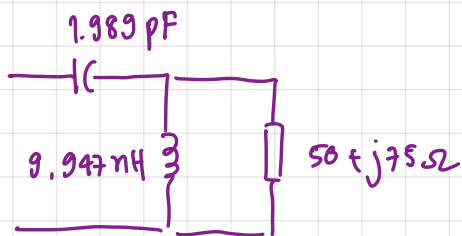
$$L_{\text{shunt}} = \frac{x Z_0}{2\pi f} = \frac{3 \times 50}{2\pi \times 2.4 \times 10^9} = 9.947 \text{ nH}$$



# The Complete Smith Chart

